

# **DRONACHARYA** Group of Institutions

## **ELECTRONIC DEVICES LABORATORY MANUAL**

**B.TECH SEMESTER –III**

**Subject Code [BEC351]**

**Session: 2024-25, Odd Semester**

<b>Name:</b>	
<b>Roll. No.:</b>	
<b>Group /Branch:</b>	

**DRONACHARYA GROUP OF INSTITUTIONS  
DEPARTMENT OF ECE  
#27 KNOWLEDGE PARK 3**

**GREATER NOIDA**

**AFFILATED TO Dr. ABDUL KALAM TECHNICAL UNIVERSITY,  
LUCKNOW**

## **Table of Contents**

1. Vision and Mission of the Institute
2. Vision and Mission of the Department
3. Programme Educational Objectives (PEOs)
4. Programme Outcomes (POs)
5. Programme Specific Outcomes (PSOs)
6. University Syllabus
7. Course Outcomes (COs)
8. CO- PO and CO-PSO mapping
9. Course Overview
10. List of Experiments
11. DOs and DON'Ts
12. General Safety Precautions
13. Guidelines for students for report preparation
14. Lab assessment criteria
15. Details of Conducted Experiments
16. Lab Experiments

## Vision and Mission of the Institute

### **Vision:**

Instilling core human values and facilitating competence to address global challenges by providing Quality Technical Education.

### **Mission:**

- **M1** - Enhancing technical expertise through innovative research and education, fostering creativity and excellence in problem-solving.
- **M2** - Cultivating a culture of ethical innovation and user-focused design, ensuring technological progress enhances the well-being of society.
- **M3** - Equipping individuals with the technical skills and ethical values to lead and innovate responsibly in an ever-evolving digital landscape.

## Vision and Mission of the Department

### **VISION**

To achieve excellence in Electronics and Computer engineering through quality education, research contributing to the emerging technologies and innovation to serve industry and society.

### **MISSION**

- **M1:** To help students achieve their goals by recognizing, identifying, and to bring up their unique strengths through quality education and cutting-edge research training.
- **M2:** To facilitate adequate exposure to the students through training in the state-of-the-art technologies.
- **M3:** To imbibe ability in the students to solve real life problems as per need of the society through nurturing their skills, creative thinking, and research acumen.

## Programme Educational Objectives (PEOs)

**PEO 1.**

To develop a strong foundation of engineering fundamentals to build successful careers maintaining high ethical standards.

**PEO 2.**

To prepare graduates for higher studies and research activities, facilitating a commitment to lifelong learning.

**PEO 3.**

To prepare graduates for higher studies and research activities, facilitating a commitment to lifelong learning.

## Programme Outcomes (POs)

- PO1: Engineering knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
- PO2: Problem analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
- PO3: Design/development of solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
- PO4: Conduct investigations of complex problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
- PO5: Modern tool usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
- PO6: The engineer and society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
- PO7: Environment and sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
- PO8: Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of engineering practice.
- PO 9: Individual and teamwork:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
- PO10: Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
- PO11: Project management and finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
- PO12: Life-long learning:** Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

## Program Specific Outcomes (PSOs)

### **PSO1:**

To analyse electronics systems applying principles of mathematics and engineering sciences, to develop innovative ethical solutions to complex engineering problems with team spirit and social commitment.

### **PSO2:**

To develop solution for real world problems based on principles of computer hardware, advanced software and simulation tools with a focus to devise indigenous, eco-friendly and energy efficient projects.

## University Syllabus

KEC351	Electronic Devices Lab	0L:0T:2P	1 Credits
--------	------------------------	----------	-----------

### SUGGESTIVE LIST OF EXPERIMENTS

1. **Study of Lab Equipment and Components:** CRO, multimeter, and function generator, power supply- active, passive components and bread board.
2. **P-N Junction diode:** Characteristics of PN junction diode - static and dynamic resistance measurement from graph.
3. **Applications of PN Junction diode:** Half & Full wave rectifier- Measurement of  $V_{rms}$ ,  $V_{dc}$ , and ripple factor.
4. **Characteristics of Zener diode:** V-I characteristics of Zener diode, graphical measurement of forward and reverse resistance.
5. **Characteristics of Photo diode:** V-I characteristics of photo diode, graphical measurement of forward and reverse resistance.
6. **Characteristics of Solar cell:** V-I characteristics of solar cell, graphical measurement of forward and reverse resistance.
7. **Application of Zener diode:** Zener diode as voltage regulator. Measurement of percentage regulation by varying load resistor.
8. **Characteristic of BJT:** BJT in CE configuration- graphical measurement of h-parameters from input and output characteristics. Measurement of  $A_v$ ,  $A_i$ ,  $R_o$  and  $R_i$  of CE amplifier with potential divider biasing.
9. **Field Effect Transistors:** Single stage common source FET amplifier –plot of gain in dB Vs frequency, measurement of, bandwidth, input impedance, maximum signal handling capacity (MSHC) of an amplifier.
10. **Metal Oxide Semiconductor Field Effect Transistors:** Single stage MOSFET amplifier –plot of gain in dB Vs frequency, measurement of, bandwidth, input impedance, maximum signal handling capacity (MSHC) of an amplifier.
11. Simulation of amplifier circuits studied in the lab using any available simulation software and measurement of bandwidth and other parameters with the help of simulation software.

### Course outcomes:

At the end of this course students will demonstrate the ability to:

1. Understand working of basic electronics lab equipment.
  2. Understand working of PN junction diode and its applications.
  3. Understand characteristics of Zener diode.
  4. Design a voltage regulator using Zener diode.
  5. Understand working of BJT, FET, MOSFET and apply the concept in designing of amplifiers.
-

Experiments available on virtual lab

P-N Junction on diode: Characteristics of Junction diode - Static and dynamic resistance measurement from graph.	<a href="http://vlabs.iitkgp.ernet.in/be/exp5/index.html">http://vlabs.iitkgp.ernet.in/be/exp5/index.html</a>
Applications of PN Junction diode: Half & Full wave rectifier-Measurement of $V_{rms}$ , $V_{dc}$ , and ripple factor.	<a href="http://vlabs.iitkgp.ernet.in/be/exp6/index.html">http://vlabs.iitkgp.ernet.in/be/exp6/index.html</a> <a href="http://vlabs.iitkgp.ernet.in/be/exp7/index.html">http://vlabs.iitkgp.ernet.in/be/exp7/index.html</a>
Characteristics of Zener diode: V-I characteristics of Zener diode, Graphical measurement of forward and reverse resistance.	<a href="http://vlabs.iitkgp.ernet.in/be/exp10/index.html">http://vlabs.iitkgp.ernet.in/be/exp10/index.html</a>
Characteristic of BJT: BJT in CE configuration.	<a href="http://vlabs.iitkgp.ernet.in/be/exp11/index.html">http://vlabs.iitkgp.ernet.in/be/exp11/index.html</a>
To study Operational Amplifier as Adder and Subtractor	<a href="http://vlabs.iitkgp.ernet.in/be/exp17/index.html">http://vlabs.iitkgp.ernet.in/be/exp17/index.html</a> <a href="http://vlabs.iitkgp.ernet.in/be/exp18/index.html">http://vlabs.iitkgp.ernet.in/be/exp18/index.html</a>



## Course Outcomes (COs)

Upon successful completion of the course, the students will be able to:

CO-1	Understand working of basic electronics lab equipment.
CO-2	Understand working of PN junction diode and its applications
CO-3	Understand characteristics of Zener diode.
CO-4	Design a voltage regulator using Zener diode.
CO-5	Understand working of BJT, FET, MOSFET and apply the concept in designing of amplifiers

## CO-PO Mapping

	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
<b>CO1</b>	2	3	2	3	3	2	3	2	1	2	3	2
<b>CO2</b>	1	2	3	2	2	2	2	3	1	3	2	2
<b>CO3</b>	2	3	2	3	2	3	3	2	2	3	2	2
<b>CO4</b>	2	3	2	3	2	2	2	2	2	2	2	2
<b>CO5</b>	2	3	2	3	2	2	3	3	1	3	3	2
<b>Course Correlation mapping</b>	<b>2</b>	<b>3</b>	<b>2</b>	<b>3</b>	<b>2</b>	<b>2</b>	<b>3</b>	<b>2</b>	<b>1</b>	<b>3</b>	<b>2</b>	<b>2</b>

**Correlation Levels: High-3, Medium-2, Low-1**

## CO-PSO Mapping

	<b>PSO1</b>	<b>PSO2</b>	<b>PSO3</b>
<b>CO1</b>	2	3	2
<b>CO2</b>	2	3	2
<b>CO3</b>	2	3	2
<b>CO4</b>	2	3	2
<b>CO5</b>	2	3	2
<b>Course Correlation mapping</b>	<b>2</b>	<b>3</b>	<b>2</b>

## Course Overview

In this lab students will study about the basics of different kinds of diodes like PN junction diode, zener diode, clipper and clampers etc. Additionally, BJT and FET along with its various configurations. Study of Half wave and full wave rectifiers using with or without filters. Measurement of Op-Amp parameters: Common mode gain, differential mode gain, CMRR, slew rate. Applications of Op-Amp: Op-Amp as summing amplifier, difference amplifier, integrator and differentiator. Field effect transistors: Single stage common source FET amplifier –plot of gain in dB Vs frequency.

## List of Experiments mapped with COs

S. No	Aim of the	COs
1.	Study of Lab Equipment and Components: CRO, multimeter, and function generator, power supply- active, passive components and bread board	<b>CO1</b>
2.	P-N Junction diode: Characteristics of PN junction diode - static and dynamic resistance measurement from graph.	<b>CO2</b>
3.	Applications of PN Junction diode: Half & Full wave rectifier- Measurement of Vrms, Vdc, and ripple factor	<b>CO2</b>
4.	Characteristics of Zener diode: V-I characteristics of Zener diode, graphical measurement of forward and reverse resistance.	<b>CO3</b>
5.	Characteristics of Photo diode: V-I characteristics of photo diode, graphical measurement of forward and reverse resistance	<b>CO2</b>
6.	Characteristics of Solar cell: V-I characteristics of solar cell, graphical measurement of forward and reverse resistance.	<b>CO2</b>
7.	Application of Zener diode: Zener diode as voltage regulator. Measurement of percentage regulation by varying load resistor.	<b>CO4</b>
8.	Characteristic of BJT: BJT in CE configuration- graphical measurement of h parameters from input and output characteristics. Measurement of Av, AI, Ro and Ri of CE amplifier with potential divider biasing.	<b>CO5</b>
9.	Field Effect Transistors: Single stage common source FET amplifier –plot of gain in dB Vs frequency, measurement of, bandwidth, input impedance, maximum signal handling capacity (MSHC) of an amplifier.	<b>CO5</b>

10.	Metal Oxide Semiconductor Field Effect Transistors: Single stage MOSFET amplifier –plot of gain in dB Vs frequency, measurement of, bandwidth, input impedance, maximum signal handling capacity (MSHC) of an amplifier	<b>CO5</b>
11.	Simulation of amplifier circuits studied in the lab using any available simulation software and measurement of bandwidth and other parameters with the help of simulation software.	<b>CO5</b>

## **DOs and DON'Ts**

1. Treat every electrical device like it is energized, even if it does not look like it is plugged in or operational.
2. Unplug appliances before performing any service or repairs on them.
3. When working on electrical devices, only use tools that have official “non-conducting” handles.
4. Try to limit the use of electrical equipment in rooms that are very cold or have a lot of condensation.
5. When handling electrical equipment, make sure your hands are dry.
6. If you spill any kind of liquid on electrical equipment, first immediately shut off power to the equipment via the main switch or circuit breaker and then unplug the equipment itself.
7. Keep all electrical circuit contact points enclosed.

## **DON'Ts**

1. First and foremost – don't touch active electrical circuits.
2. Never touch electrical equipment when any part of your body is wet, (that includes fair amounts of perspiration).
3. Do not store liquids of any sort near electrical equipment.
4. If a person comes into contact with an energized electrical conductor, do not touch the equipment, its cords, or the person affected because the charge may pass to you. Instead, shut down the main power source via the circuit breaker and then unplug the equipment using a leather belt.
5. Do not wear metal of any sort if you are working on electrical equipment.
6. Also, do not try to poke, probe, or fix electrical equipment with objects like pencils or rulers because the metal in them can serve as a form of conductor.

## General Safety Precautions

### Precautions (In case of Injury or Electric Shock)

1. To break the victim with live electric source, use an insulator such as firewood or plastic to break the contact. Do not touch the victim with bare hands to avoid the risk of electrifying yourself.
2. Unplug the risk of faulty equipment. If the main circuit breaker is accessible, turn the circuit off.
3. If the victim is unconscious, start resuscitation immediately, use your hands to press the chest in and out to continue breathing function. Use mouth-to-mouth resuscitation if necessary.

### Precautions (In case of Fire)

1. Turn the equipment off. If the power switch is not immediately accessible, take plug off.
2. If fire continues, try to curb the fire if possible, by using the fire extinguisher or by covering it with a heavy cloth if possible isolate the burning equipment from the other surrounding equipment.
3. Sound the fire alarm by activating the nearest alarm switch located in the hallway.
4. Call security and emergency department immediately:

**Emergency : 201 (Reception)**  
**Security : 231 (Gate No.1)**

## Guidelines to Students for Report Preparation

All students are required to maintain a record of the experiments conducted by them. Guidelines for its preparation are as follows:-

- 1) All files must contain a title page followed by an index page. *The files will not be signed by the faculty without an entry in the index page.*
- 2) Student's Name, Roll number and date of conduction of experiment must be written on all pages.
- 3) For each experiment, the record must contain the following
  - (i) Aim/Objective of the experiment
  - (ii) Pre-experiment work (as given by the faculty)
  - (iii) Lab assignment questions and their solutions
  - (iv) Test Cases (if applicable to the course)
  - (v) Results/ output

**Note:**

1. Students must bring their lab record along with them whenever they come for the lab.
2. Students must ensure that their lab record is regularly evaluated.

## Lab Assessment Criteria

An estimated 10 lab classes are conducted in a semester for each lab course. These lab classes are assessed continuously. Each lab experiment is evaluated based on 5 assessment criteria as shown in following table. Assessed performance in each experiment is used to compute Course Outcomes attainment as well as internal marks in the lab course.

<b>Grading Criteria</b>	<b>Exemplary (4)</b>	<b>Competent (3)</b>	<b>Needs Improvement (2)</b>	<b>Poor (1)</b>
<b>AC1:</b> Designing experiments	The student chooses the problems to explore.	The student chooses the problems but does not set an appropriate goal as how to explore.	Student fails to define the problem adequately	Student does not identify the problem
<b>AC2:</b> Collecting data through observation and/or experimentation	Develops a clear procedure for investigating the problem	Observations are completed with necessary theoretical calculations and proper identification of required components.	Observations are completed with necessary theoretical calculations but without proper understanding. Obtain the correct values for only few components after calculations. Followed the given experimental procedures, but obtained results with some errors	Observations are incomplete. Lacks the appropriate knowledge of the lab procedures.
<b>AC3:</b> Interpreting data	Decides what data and observations are to be collected and verified	Can decide what data and observations are to be collected but lacks the knowledge to verify	Student decides what data to gather but not sufficient	Student has no knowledge of what data and observations are to be collected
<b>AC4:</b> Drawing conclusions	Interprets and analyses the data in order to propose viable conclusions and solutions	Incomplete analysis of data hence the quality of conclusions drawn is not up to the mark	Cannot analyse the data or observations for any kind of conclusions	Lacks required knowledge to propose viable conclusions and solutions
<b>AC5:</b> Lab record assessment	Well-organized and confident presentation of record & able to correlate the theoretical concepts with the concerned lab results with appropriate reasons.	Presentation of record acceptable	Presentation of record lacks clarity and organization	No efforts exhibited



# LAB EXPERIMENTS

**EXPERIMENT NO. – 1**

**OBJECTIVE:** Study of Lab Equipment and Components: CRO, multimeter, and function generator, power supply- active, passive components and bread board.

**APPARATUS REQUIRED:**CRO, Function generator and probes, multimeter, and function generator, power supply- active, passive components and bread board.

**THEORY:**

C.R.O. (Cathode Ray Oscilloscope) is the instrument which is used to observe signal waveforms. Signals are displayed in time domain i.e. variation in amplitude of the signal with respect to time is plotted on the CRO screen. X-axis represents time and Y-axis represents amplitude. It is used to measure amplitude, frequency and phase of the waveforms. It is also used to observe shape of the waveform. C.R.O. is useful for troubleshooting purpose. It helps us to find out gain of amplifier, test oscillator circuits. We can measure amplitude and frequency of the waveforms at the different test points in our circuit. Thus, it helps us for fault finding procedure. In dual channel C.R.O. X-Y mode is available which is used to create patterns. Latest digital storage oscilloscope display voltage and frequency directly on the LCD and does not require any calculations. It can also store waveform for further analysis. More detailed study on C.R.O. will be covered in EMI laboratory (SEM-V). In this practical, we will measure amplitude and frequency of the different waveforms like sine wave, square wave, triangular wave and ramp wave.

**PROCEDURE**

1. Understand the significance of each and every knob on the CRO.
2. From the given function generator feed in a sinusoidal wave and adjust the time base knob and the amplitude knob to observe the waveform as a function of time.
3. Measure the time period and amplitude (peak to peak) of the signal. Find the frequency and verify if the same frequency is given from the function generator.
4. Observe two waveforms simultaneously on the two channels of a CRO.
5. Repeat the above steps for pulse and triangular waveforms.
6. Report the readings and the waveforms taken.

**MEASUREMENTS:**

Amplitude = no. of vertical divisions \* Volts/div.

Time period = no. of horizontal divisions \* Time/div.

Frequency=(1/T)Hz

**MODEL GRAPHS:**

 


Figure: 1.1 Graph of Sine wave in CRO Screen

**APPLICATIONS OF CRO:**

1. Measurement of current
2. Measurement of voltage
3. Measurement of power
4. Measurement of frequency
5. Measurement of phase angle
6. To see transistor curves
7. To trace and measuring signals of RF, IF and AF in radio and TV.
8. To trace visual display of sine waves.

Observation table:

Function	Vertical Division (a)	Volt/div (b)	Amplitude (p-p) $V=a*b$	Horizontal Div (c)	Time/div (d)	Time T $=c*d$	Freq. $F=1/T$
Sine wave							
Square Wave							
Triangular Wave							
Ramp Wave							

Draw observed waveforms:

Sine wave: (Amplitude : \_\_\_\_\_ Frequency: \_\_\_\_\_ )


**ELECTRONIC DEVICES LAB (BEC351)**

---

Square wave: (Amplitude : \_\_\_\_\_ Frequency: \_\_\_\_\_ )


Triangular wave: (Amplitude : \_\_\_\_\_ Frequency: \_\_\_\_\_ )


Ramp: ((Amplitude : \_\_\_\_\_ Frequency: \_\_\_\_\_ )


**Result:** Thus, studied the whole characteristics of CRO and plotted the waveforms

## EXPERIMENT 2

**OBJECTIVE:** P-N Junction diode: Characteristics of PN junction diode - static and dynamic resistance measurement from graph.

**APPARATUS REQUIRED:**

- P-N Diode 1N4007
- Regulated Power supply (0-15V)
- Resistor  $1K\Omega$
- Ammeters (0-200mA, 0-200 $\mu$ A)
- Voltmeter (0-20V)
- Breadboard Connecting wires

**THEORY:**

The semiconductor diode is formed by doping P-type impurity in one side and N-type of impurity in another side of the semiconductor crystal forming a p-n junction as shown in the following figure.

 


Figure:2.1 Construction of Depletion region

At the junction initially free charge carriers from both side recombine forming negatively charged ions in P side of junction(an atom in P-side accept electron and becomes negatively charged ion) and positively charged ion on n side(an atom in n-side accepts hole i.e. donates electron and becomes positively charged ion)region. This region deplete of any type of free charge carrier is called as depletion region. Further recombination of free carrier on both side is prevented because of the depletion voltage generated due to charge carriers kept at distance by depletion (acts as a sort of insulation) layer as shown dotted in the above figure.

**Working principle:**

When voltage is not applied across the diode, depletion region forms as shown in the above figure. When the voltage is applied between the two terminals of the diode (anode and cathode) two possibilities arises depending on polarity of DC supply.

[1] Forward-Bias Condition: When the +Ve terminal of the battery is connected to P-type material & -Ve terminal to N-type terminal as shown in the circuit diagram, the diode is said to be forward biased. The application of forward bias voltage will force electrons in N-type and holes in P-type material to recombine with the ions near boundary and to flow crossing junction. This reduces width of depletion region. This further will result in increase in majority carriers flow across the junction. If forward bias is

further increased in magnitude the depletion region width will continue to decrease, resulting in exponential rise in current as shown in ideal diode characteristic curve.

[2] Reverse-biased: If the negative terminal of battery (DC power supply) is connected with P-type terminal of diode and +Ve terminal of battery connected to N type then diode is said to be reverse biased. In this condition the free charge carriers (i.e. electrons in N-type and holes in P-type) will move away from junction widening depletion region width. The minority carriers (i.e. -ve electrons in p-type and +ve holes in n-type) can cross the depletion region resulting in minority carrier current flow called as reverse saturation current( $I_s$ ). As no of minority carrier is very small so the magnitude of  $I_s$  is few microamperes. Ideally current in reverse bias is zero.

In short, current flows through diode in forward bias and does not flow through diode in reverse bias. Diode can pass current only in one direction.

 
**CIRCUIT DIAGRAM:****FORWARD BIAS:**

Figure: 2.2 Circuit diagram of forward bias of PN junction

REVERSE BIAS:

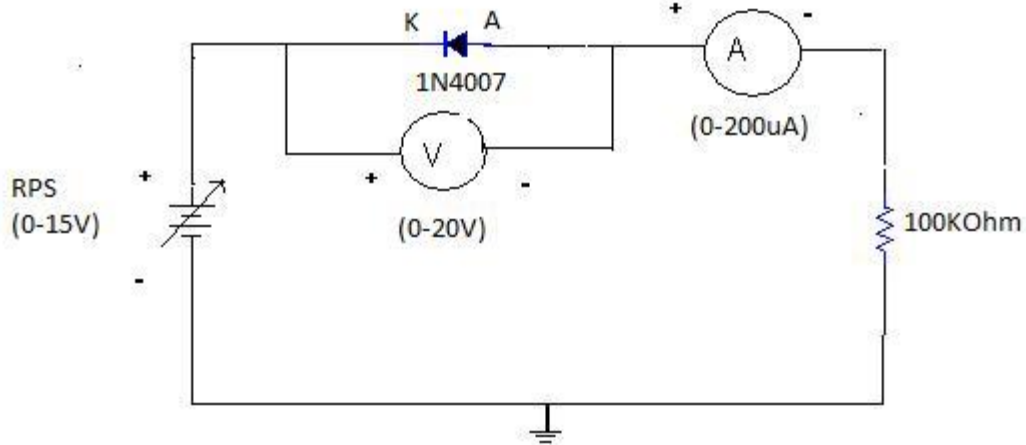


Figure: 2.3 Circuit diagram of Reverse bias of PN junction

MODEL GRAPH:

 


Figure: 2.4 Graph of VI characteristics of forward bias and Reverse bias of PN junction



**PROCEDURE:**

**FORWARD BIAS:**

1. Connections are made as per the circuit diagram.
2. For forward bias, the RPS +ve is connected to the anode of the diode and RPS –ve is connected to the cathode of the diode,
3. Switch on the power supply and increases the input voltage (supply voltage) in steps.
4. Note down the corresponding current flowing through the diode and voltage across the diode for each and every step of the input voltage.
5. The reading of voltage and current are tabulated.
6. Graph is plotted between voltage and current.

**OBSERVATIONS:**

S.NO	$V_f$ (V)	$I_f$ (mA)

**PROCEDURE:**

**REVERSE BIAS:**

7. Connections are made as per the circuit diagram.
8. For reverse bias, the RPS +ve are connected to the cathode of the diode and RPS -ve is connected to the anode of the diode.
9. Switch on the power supply and increase the input voltage (supply voltage) in steps
10. Note down the corresponding current flowing through the diode voltage across the diode for each and every step of the input voltage.
11. The readings of voltage and current are tabulated
12. Graph is plotted between voltage and current.

**OBSEVATIONS:**

S.NO	$V_r$ (V)	$I_r$ (mA)

**RESULT:** Forward and Reverse Bias characteristics for a p-n diode is observed

### EXPERIMENT 3

**OBJECTIVE:** Application of Zener diode: Zener diode as voltage regulator. Measurement of percentage regulation by varying load resistor.

**APPARATUS REQUIRED:**


- Zener diode – ECZ5V1
- Regulated Power Supply (0-15V)
- Voltmeter (0-20V)
- Ammeter (0-200mA)
- Resistor (1K $\Omega$ )
- Breadboard
- Connecting wires

**THEORY:**

A zener diode is heavily doped p-n junction diode, specially made to operate in the break down region. A p-n junction diode normally does not conduct when reverse biased. But if the reverse bias is increased, at a particular voltage it starts conducting heavily. This voltage is called Break down Voltage. High current through the diode can permanently damage the device. To avoid high current, we connect a resistor in series with zener diode. Once the diode starts conducting it maintains almost constant voltage across the terminals whatever may be the current through it, i.e., it has very low dynamic resistance. It is used in voltage regulators.

**CIRCUIT DIAGRAM:**

SUPPLY SIDE:

 

---

Figure: 3.1 Circuit diagram of Zener diode work as Voltage regulators.

LOAD SIDE:

 


Figure: 3.2 Circuit diagram of Zener diode work as Voltage regulators.

**PROCEDURE:**

SUPPLY SIDE:

9. Connections are made as per the circuit diagram.
10. The Regulated power supply voltage is increased in steps.
11. For different input voltages ( $V_i$ ) corresponding output voltages ( $V_o$ ) are observed and then noted in the tabular form.
12. A graph is plotted between input voltage ( $V_i$ ) and the output voltage ( $V_o$ ).

LOAD SIDE:

1. Connection are made as per the circuit diagram
2. The load is placed in full load condition and the output voltage ( $V_o$ ), load current ( $I_L$ ) are measured.
3. The above step is repeated by decreasing the value of the load in steps.
4. All the readings are tabulated and a graph is plotted between load current ( $I_L$ ) and the output voltage ( $V_o$ ).

**OBSERVATIONS:-**

SUPPLY SIDE:-

S.NO	$V_i$ (V)	$V_o$ (V)

LOAD SIDE:-

S.NO	$I_L$ (V)	$V_o$ (V)

**MODEL GRAPH:**

SUPPLY SIDE:

LOAD SIDE

 


Figure: 3.3 Graph of Zener diode work as Voltage regulators.

**RESULT:** Regulator characteristics of zener diode are obtained and graphs are plotted for load and supply side.

## EXPERIMENT 4

**OBJECTIVE:** Applications of PN Junction diode: Half & Full wave rectifier- Measurement of  $V_{rms}$ ,  $V_{dc}$ , and ripple factor.

**APPARATUS REQUIRED:**

AC Supply 12V

PN Diode, 1N4007

Capacitor, 470 $\mu$ F

Variable Resistor (0-10) K $\Omega$

Connecting wires

Breadboard

Multimeter

**THEORY:**

During positive half-cycle of the input voltage, the diode D1 is in forward bias and conducts through the load resistor R1. Hence the current produces an output voltage across the load resistor R1, which has the same shape as the +ve half cycle of the input voltage. During the negative half-cycle of the input voltage, the diode is reverse biased and there is no current through the circuit. i.e., the voltage across R1 is zero.

The net result is that only the +ve half cycle of the input voltage appears across the load. The average value of the half wave rectified o/p voltage is the value measured on dc voltmeter. For practical circuits, transformer coupling is usually provided for two reasons.

1. The voltage can be stepped-up or stepped-down, as needed.
2. The ac source is electrically isolated from the rectifier. Thus preventing shock hazards in the secondary circuit.

**CIRCUIT DIAGRAMS:**

WITHOUT FILTER:

 


Figure: 4.1 Circuit diagram of Half wave rectifier

WITH FILTER:

 


Figure: 4.2 Circuit diagram of Half wave rectifier with filter.

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. Connect the primary side of the transformer to ac mains and the secondary side to the rectifier input.
3. By the multimeter, measure the ac input voltage of the rectifier and, ac and dc voltage at the output of the rectifier.
4. Find the theoretical of dc voltage by using the formula,

$$V_{dc} = V_m / \pi$$

Where,  $V_m = 2V_{rms}$ , ( $V_{rms}$ =output ac voltage.)

The Ripple factor is calculated by using the formula

$r = \text{ac output voltage} / \text{dc output voltage}$ .

**REGULATION CHARACTERSTICS:**

1. Connections are made as per the circuit diagram.
2. By increasing the value of the rheostat, the voltage across the load and current flowing through the load are measured.
3. The reading is tabulated.

---

## ELECTRONIC DEVICES LAB (BEC351)

---

4. Draw a graph between load voltage ( $V_L$ ) and load current ( $I_L$ ) taking  $V_L$  on X-axis and  $I_L$  on y-axis
5. From the value of no-load voltages, the % regulation is calculated using the formula,

### OBSERVATIONS:

WITHOUT FILTER:

$R_L$ ( $K\Omega$ )	$V_{ac}$ (Volts)	$V_{dc}$ (Volts)	Ripple Factor $= V_{ac}/ V_{dc}$	% Regulation $(V_{NL}-V_{FL})/V_{FL} *100$

WITH FILTER:

$R_L$ ( $K\Omega$ )	$V_{ac}$ (Volts)	$V_{dc}$ (Volts)	Ripple Factor $= V_{ac}/ V_{dc}$	% Regulation $(V_{NL}-V_{FL})/V_{FL} *100$



**MODEL GRAPHS:**

**HALFWAVE RECTIFIER (WITH & WITHOUT FILTER):**

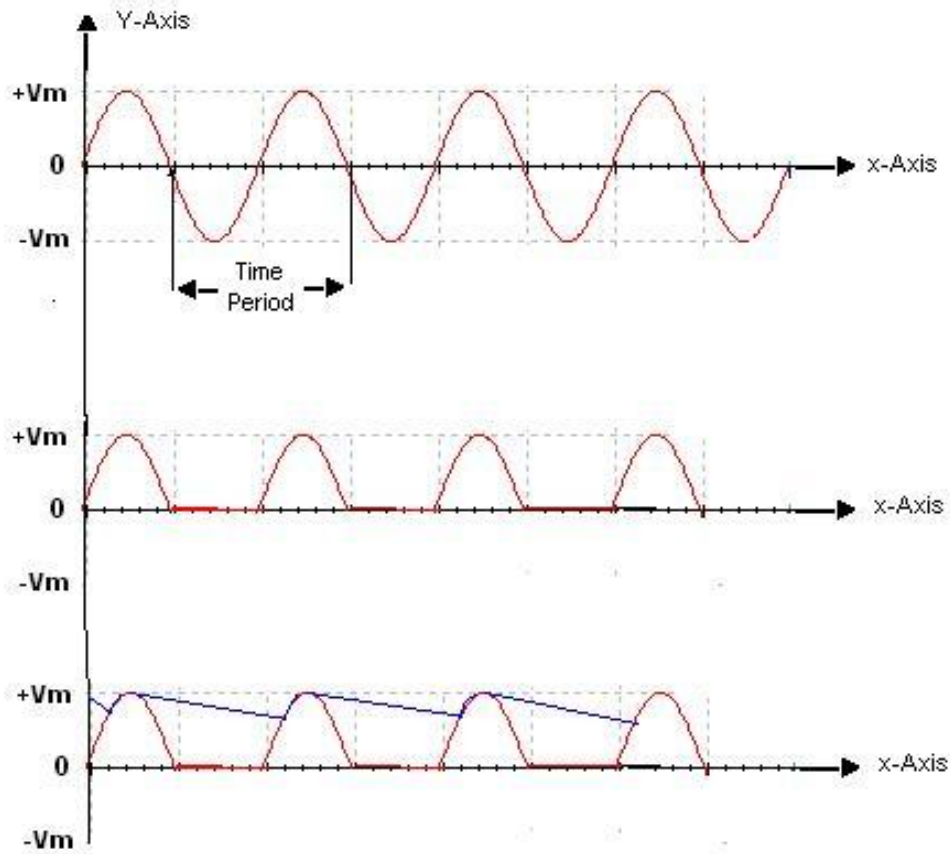


Figure: 4.3 Graph of Half wave rectifier

**RESULT:** The Ripple factor and % regulation for the Half-wave Rectifier with and without filters is measured.

## EXPERIMENT 5

**OBJECTIVE:** To find the Ripple factor and regulation of a Full-wave Rectifier with and without filter.

**APPARATUS REQUIRED:**

AC Supply (12V-0-12V)

PN Diodes 1N4007

Capacitor 470 $\mu$ F

Connecting Wires

Variable resistor (0-10) K $\Omega$

Breadboard

Multimeter

**THEORY:**

The circuit of a center-tapped full wave rectifier uses two diodes D1&D2. During positive half cycle of secondary voltage (input voltage), the diode D1 is forward biased and D2 is reverse biased. The diode D1 conducts and current flows through load resistor  $R_L$ . During negative half cycle, diode D2 becomes forward biased and D1 reverse biased. Now, D2 conducts and current flows through the load resistor  $R_L$  in the same direction. There is a continuous current flow through the load resistor  $R_L$ , during both the half cycles and will get unidirectional current as show in the model graph. The difference between full wave and half wave rectification is that a full wave rectifier allows unidirectional (one way) current to the load during the entire 360 degrees of the input signal and half-wave rectifier allows this only during one half cycle (180 degree).

**CIRCUIT DIAGRAM:**

WITHOUT FILTER:

 


Figure: 5.1 Circuit diagram of full wave rectifier without filter

WITH FILTER:

 


Figure: 5.2 Circuit diagram of Full wave rectifier with filter

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. Connect the ac mains to the primary side of the transformer and the secondary side to the rectifier.
3. Measure the ac voltage at the input side of the rectifier.
4. Measure both ac and dc voltages at the output side the rectifier.
5. Find the theoretical value of the dc voltage by using the formula  $V_{dc}=2V_m/\pi$
6. Connect the filter capacitor across the load resistor and measure the values of  $V_{ac}$  and  $V_{dc}$  at the output.
7. The theoretical values of Ripple factors with and without capacitor are calculated.
8. From the values of  $V_{ac}$  and  $V_{dc}$  practical values of Ripple factors are calculated. The practical values are compared with theoretical values.

**OBSERVATIONS:**

WITHOUT FILTER:

$R_L$ (Ohms)	$V_{ac}$ (Volts)	$V_{dc}$ (Volts)	Ripple Factor = $V_{ac}/V_{dc}$	% Regulation $(V_{NL}-V_{FL})/V_{FL} * 100$
-----------------	---------------------	---------------------	------------------------------------	--

--	--	--	--	--

WITH FILTER:

$R_L$ (Ohms)	$V_{ac}$ (Volts)	$V_{dc}$ (Volts)	Ripple Factor $= V_{ac} / V_{dc}$	% Regulation $(V_{NL} - V_{FL}) / V_{FL} * 100$

**MODEL GRAPHS:**

FULLWAVE RECTIFIER (WITH & WITHOUT FILTER):

 


Figure: 5.3 Graph of Full wave rectifier with filter

**RESULT:**

The ripple factor of the Full-wave rectifier (with filter and without filter) is calculated.

**EXPERIMENT 6**

**OBJECTIVE:** 1.To observe and draw the input and output characteristics of a transistor connected in common base configuration.

2. To find  $\alpha$  of the given transistor.

**APPARATUS REQUIRED:**

NAME OF THE EQUIPMENT	RANGE	QUANTITY
Transistor	BC 547	
Regulated power supply	(0-30)V	
Voltmeter	(0-20V),(0-2)V	
Ammeters	(0-50)mA,(0-50)mA	
Resistor	1K $\Omega$	
Bread board		
Connecting wires		

**THEORY:**A transistor is a three terminal active device. The terminals are emitter, base, collector. In CB configuration, the base is common to both input (emitter) and output (collector). For normal operation, the E-B junction is forward biased and C-B junction is reverse biased. With an increasing the reverse collector voltage, the space-charge width at the output junction increases and the effective base width 'W' decreases. This phenomenon is known as "Early effect". Then, there will be less chance for recombination within the base region. With increase of charge gradient with in the base region, the current of minority

carriers injected across the emitter junction increases. The current amplification factor of CB configuration is given by  $\alpha = \Delta I_C / \Delta I_E$

**PROCEDURE:**

**INPUT CHARACTERISTICS:**

1. Connections are made as per the circuit diagram.
2. For plotting the input characteristics, the output voltage  $V_{CB}$  is kept constant at 0V and for different values of  $V_{EB}$  note down the values of  $I_E$ .
3. Repeat the above step keeping  $V_{CB}$  at V, V, and V. All the readings are tabulated.
4. A graph is drawn between  $V_{EB}$  and  $I_E$  for constant  $V_{CB}$ .

**OUTPUT CHARACTERISTICS:**

1. Connections are made as per the circuit diagram.
2. For plotting the output characteristics, the input  $I_E$  is kept constant at 5mA and for different values of  $V_{CB}$ , note down the values of  $I_C$ .
3. Repeat the above step for the values of  $I_E$  at mA, mA, and mA, all the readings are tabulated.
4. A graph is drawn between  $V_{CB}$  and  $I_C$  for constant I

**PRECAUTIONS:**

1. The supply voltages should not exceed the rating of the transistor.
2. Meters should be connected properly according to their polarities.

**CIRCUIT**

**DIAGRAM:**

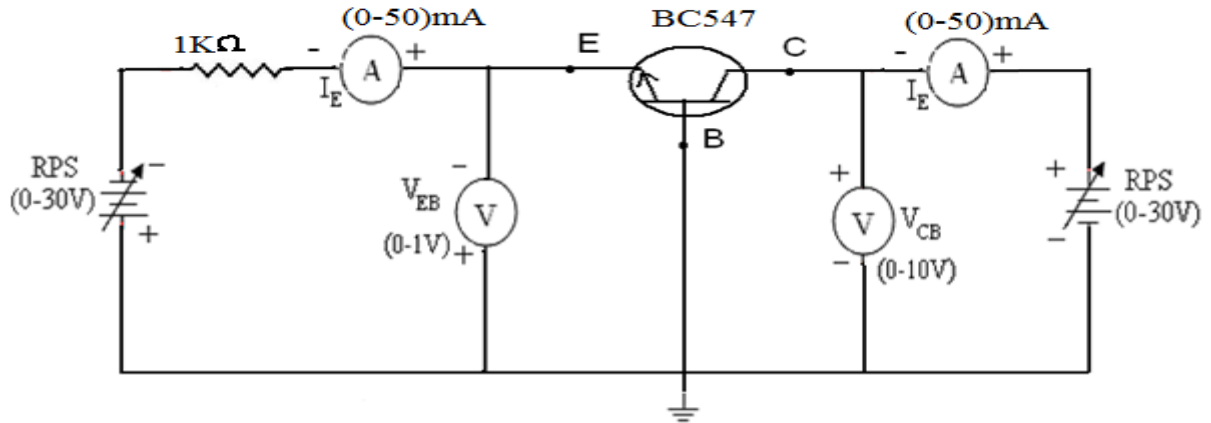


Figure: 6.1 Circuit diagram of NPN transistor in Common base configuration

**OBSERVATIONS:**

**INPUT CHARACTERISTICS:**

S.No	$V_{CB} = \quad \text{V}$		$V_{CB} = \quad \text{V}$		$V_{CB} = \quad \text{V}$	
	$V_{EB}(\text{V})$	$I_E(\text{mA})$	$V_{EB}(\text{V})$	$I_E(\text{mA})$	$V_{EB}(\text{V})$	$I_E(\text{mA})$

**OUTPUT CHARACTERISTICS:**

S.No	$I_E = \quad \text{mA}$		$I_E = \quad \text{mA}$		$I_E = \quad \text{mA}$	
	$V_{CB}(\text{V})$	$I_C(\text{mA})$	$V_{CB}(\text{V})$	$I_C(\text{mA})$	$V_{CB}(\text{V})$	$I_C(\text{mA})$

--	--	--	--	--	--	--

**CALCULATIONS:-**


**Input impedance**      =    $(\Delta V_{EB}V / \Delta I_E)\Omega$

**Output impedance**    =  $(\Delta V_{CB}V / \Delta I_C)\Omega$


**Current gain**            =  $\Delta I_C / \Delta I_E$



**Input Characteristics:**

 

**Output characteristics:**

 

---

Figure: 6.2 Input and Output VI characteristics NPN transistor in Common base configuration

**RESULT:** Thus studied the input and output characteristics of a transistor connected in common base configuration.

**EXPERIMENT 7**

**OBJECTIVE:** Characteristic of BJT: BJT in CE configuration- graphical measurement of  $h$  parameters from input and output characteristics. Measurement of  $A_v$ ,  $A_i$ ,  $R_o$  and  $R_i$  of CE amplifier with potential divider biasing.

**APPARATUS REQUIRED** : BJT Trainer kit.

NAME OF THE EQUIPMENT	RANGE	QUANTITY
Transistor	(BC 547)	
R.P.S	(0-30V)	
Voltmeters	(0-20V)	
Ammeters	(0-500) $\mu$ A, (0-50)mA	
Resistors	1K $\Omega$	
Bread board		
Connecting Wires		

**THEORY:**

A transistor is a three terminal device. The terminals are emitter, base, collector. In common emitter configuration, input voltage is applied between base and emitter terminals and output is taken across the collector and emitter terminals.

Therefore the emitter terminal is common to both input and output.

The input characteristics resemble that of a forward biased diode curve. This is expected since the Base-Emitter junction of the transistor is forward biased. As compared to CB arrangement  $I_B$  increases less rapidly with  $V_{BE}$ . Therefore input resistance of CE circuit is higher than that of CB circuit.

The output characteristics are drawn between  $I_c$  and  $V_{CE}$  at constant  $I_B$ . the collector current varies with  $V_{CE}$  upto few volts only. After this the collector current becomes almost constant, and independent of  $V_{CE}$ . The value of  $V_{CE}$  up to which the collector current changes with  $V_{CE}$



**OUTPUT CHARACTERISTICS:**

 


Figure: 7.2 Input and Output VI characteristics NPN transistor in Common emitter configuration

**PROCEDURE:**

**INPUT CHARACTERISTICS:**

1. Connect the circuit as per the circuit diagram.
2. For plotting the input characteristics the output voltage  $V_{CE}$  is kept constant at  $V$  and for different values of  $V_{BE}$ . Note down the values of  $I_C$
3. Repeat the above step by keeping  $V_{CE}$  at  $V$ .
4. Tabulate all the readings.
5. plot the graph between  $V_{BE}$  and  $I_B$  for constant  $V_{CE}$

**OUTPUT CHARACTERISTICS:**

1. Connect the circuit as per the circuit diagram
2. for plotting the output characteristics the input current  $I_B$  is kept constant at  $\mu A$  and for different values of  $V_{CE}$  note down the values of  $I_C$
3. repeat the above step by keeping  $I_B$  at  $\mu A$
4. tabulate the all the readings
5. plot the graph between  $V_{CE}$  and  $I_C$  for constant  $I_B$

**TABULAR COLUMNS:**

**INPUT CHARACTERISTICS:**

S.NO	$V_{CE} = \quad V$		$V_{CE} = \quad V$		$V_{CE} = \quad V$	
	$V_{BE}(V)$	$I_B(\mu A)$	$V_{BE}(V)$	$I_B(\mu A)$	$V_{BE}(V)$	$I_B(\mu A)$

**OUTPUT CHARACTERISTICS:**

S.NO	$I_B = \quad \mu A$		$I_B = \quad \mu A$		$I_B = \quad \mu A$	
	$V_{CE}(V)$	$I_C(mA)$	$V_{CE}(V)$	$I_C(mA)$	$V_{CE}(V)$	$I_C(mA)$

**PRECAUTIONS:**

1. The supply voltage should not exceed the rating of the transistor
2. Meters should be connected properly according to their polarities .

**RESULT:** Thus, studied the input and output characteristics of a transistor connected in common emitter configuration.

## EXPERIMENT 8

**OBJECTIVE:** Field Effect Transistors: Single stage common source FET amplifier –plot of gain in dB Vs frequency, measurement of, bandwidth, input impedance, maximum signal handling capacity (MSHC) of an amplifier..

### APPARATUS REQUIRED:

JFET (BFW11)

Regulated Power Supply (0-15V)

Voltmeter (0-20V)

Ammeter (0-200mA)

Breadboard

Connecting wires

### THEORY:

A FET is a three terminal device, having the characteristics of high input impedance and less noise, the Gate to Source junction of the FET is always reverse biased. In response to small applied voltage from drain to source, the n-type bar acts as sample resistor, and the drain current increases linearly with  $V_{DS}$ . With increase in  $I_D$  the ohmic voltage drop between the source and the channel region reverse biases the junction and the conducting position of the channel begins to remain constant. The  $V_{DS}$  at this instant is called “pinch of voltage”.

If the gate to source voltage ( $V_{GS}$ ) is applied in the direction to provide additional reverse bias, the pinch off voltage will be decreased. In amplifier application, the FET is always used in the region beyond the pinch-off.

$$I_{DS} = I_{DSS}(1 - V_{GS}/V_P)^2$$

**CIRCUIT DIAGRAM:**

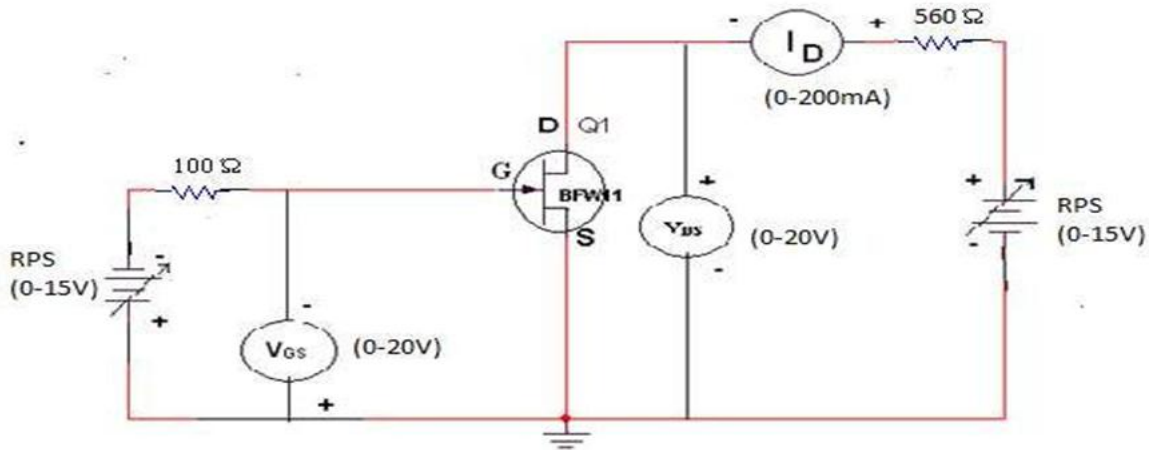


Figure: 8.1 Circuit diagram of FET in Common source Configuration

**PROCEDURE:**

1. All the connections are made as per the circuit diagram.
2. To plot the drain characteristics, keep  $V_{GS}$  constant at 0V.
3. Vary the  $V_{DD}$  and observe the values of  $V_{DS}$  and  $I_D$ .
4. Repeat the above steps 2, 3 for different values of  $V_{GS}$  at 0.1V and 0.2V.
5. All the readings are tabulated.
6. To plot the transfer characteristics, keep  $V_{DS}$  constant at 1V.
7. Vary  $V_{GG}$  and observe the values of  $V_{GS}$  and  $I_D$ .
8. Repeat steps 6 and 7 for different values of  $V_{DS}$  at 1.5 V and 2V.
9. The readings are tabulated.

**OBSERVATIONS:**

**DRAIN CHARACTERISTICS:**


S.NO	$V_{GS}=0V$		$V_{GS}=-1V$		$V_{GS}=-2V$	
	$V_{DS}(V)$	$I_D(mA)$	$V_{DS}(V)$	$I_D(mA)$	$V_{DS}(V)$	$I_D(mA)$

TRANSFER CHARACTERISTICS:

S.NO	$V_{DS} = 0.5V$		$V_{DS} = 1V$		$V_{DS} = 1.5V$	
	$V_{GS}$ (V)	$I_D$ (mA)	$V_{GS}$ (V)	$I_D$ (mA)	$V_{GS}$ (V)	$I_D$ (mA)

**MODEL GRAPH:**

DRAIN CHARACTERISTICS:

 

TRANSFER CHARACTERISTICS:

 


Figure: 8.2 Graph of FET in Common source Configuration

**RESULT:** The drain and transfer characteristics of a FET are drawn.



## EXPERIMENT 9

**OBJECTIVE:** To obtain characteristics of light emitting diode (LED)

**APPARATUS REQUIRED**

Led  
Connecting Leads  
Resistance  
DC Supply

**Introduction:**

LED is semiconductor junction diode which emits light when current passes through it in forward bias condition. P type of semiconductor consists of large number of holes while N type of semiconductor consists of large number of electrons. At zero bias (no voltage across junction), depletion region exists and it separate out two regions. When LED is forward biased, barrier potential reduces and depletion region becomes narrow. Electron crosses the depletion region and recombines with holes. Similarly holes crosses depletion region and recombine with electrons. Each recombination of hole and electron produces photon (light) The intensity of light emitted depends on the number of minority carriers available for recombination. Wavelength (or frequency) of emitted light depends on band-gap energy. The light emitting diode works by the process of spontaneous emission.

Light source material must have direct band gap. In a direct band gap semiconductor material electron and hole recombine directly across band gap without need of third particle to conserve momentum.

Light source materials are made from compound of group-III (Al,Ga,In) and group-V (P,As,Sb) element. The wavelength generated by the LED depends on bandgap energy and bandgap energy depends on doping level of above elements. Let us understand relation between frequency of emission and energy.

**Procedure:**

1. Connect the power supply, voltmeter, current meter with the LED as shown in the circuit diagram.
2. Increase voltage from the power supply from 0V to 20V in step as shown in the observation table
3. Measure voltage across LED and current through the LED. Note down readings in the observation table and also observe light coming from LED.
4. Reverse DC power supply polarity for reverse bias
5. Repeat the above procedure for the different values of supply voltage for reverse bias
6. Draw VI characteristics for forward bias and reverse bias in one graph

**Circuit diagram (forward bias):**

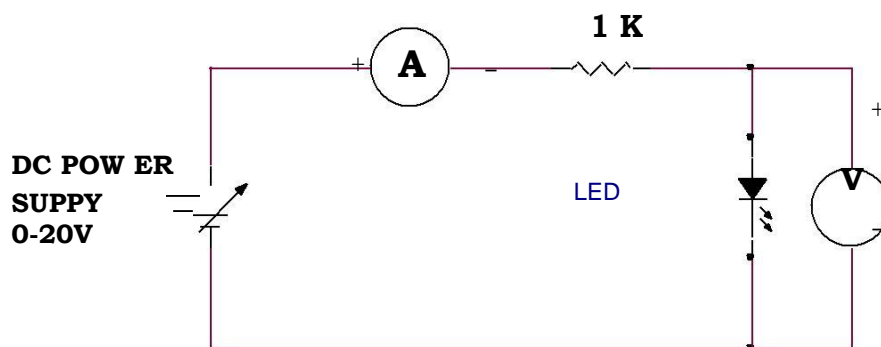


Figure :9.1 Circuit diagram of LED in forward bias

**Circuit diagram (reverse bias):**

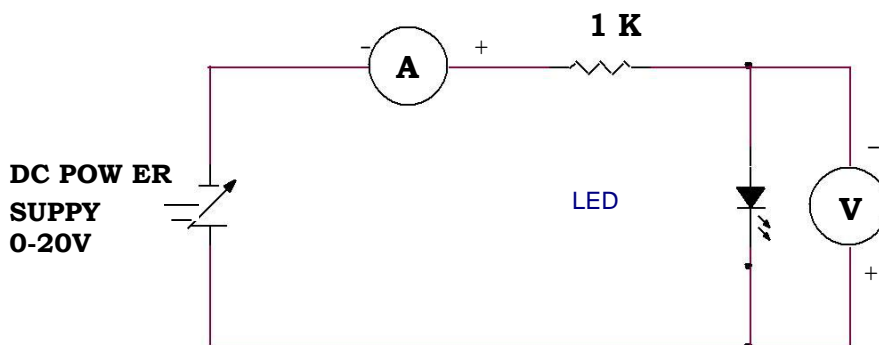


Figure :9.2 Circuit diagram of LED in Reverse bias

---

## ELECTRONIC DEVICES LAB (BEC351)

---

**Observation table: (Forward bias)**

Sr. No.	Supply voltage (Volt)	Diode voltage (Vd)	Diode current (Id)
1.	0		
2.	0.5		
3.	1		
4.	2		
5.	5		
6.	10		
7.	15		
8.	20		

**Observation table: (Reverse bias)**

Sr. No.	Supply voltage	Diode voltage (Vd)	Diode current (Id)
1.	0		
2.	2		
3.	5		
4.	10		
5.	15		
6.	20		

Result: Thus studied the characteristics of LED and plotted the graph.

This lab manual has been updated by

Ms Anuradha Yadav

Cross checked By HOD ECE

Please spare some time to provide your valuable  
feedback.