

**B TECH**  
**(SEM I) THEORY EXAMINATION 2017-18**  
**ELECTRONICS ENGINEERING**

Time: 3 Hours

Total Marks: 100


- Notes:** 1. Attempt all Sections.  
 2. Assume any missing data.

**SECTION A**

- 1. Attempt all questions in brief. 2 x 10 = 20**
- Explain bulk resistance
  - Explain up down circuit analysis
  - Define the terms conductivity, intrinsic concentration and energy gap of a semiconductor material.
  - A silicon diode has a saturation current of 5 nA at 25°C. What is the saturation current at 100°C?
  - Describe drain curves for depletion mode MOSFET.
  - Enlist the difference between JFET and BJT.
  - Draw the Capacitance versus Voltage transfer characteristic for the Varactor Diode.
  - Write the advantages of Negative Feedback in Amplifiers.
  - Draw the block diagram of four types of negative feedback amplifiers.
  - Explain how to determine phase of an unknown signal.

**SECTION B**

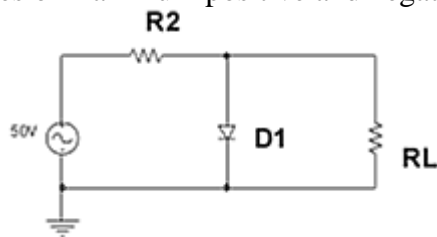
- 2. Attempt any three of the following: 10 x 3 = 30**
- Sketch the waveform output  $V_{out}$  in the circuit of the given figure indicating the values of maximum positive and negative output voltages.



- Describe and compare different types of biasing methods.
- Describe the procedure to obtain the Lissajous pattern on the screen of a CRO.
- Describe the CMOS inverter and its VTC with help of a neat sketch.
- With the help of a neat block diagram of OPAMP list and describe its major characteristics.

**SECTION C**

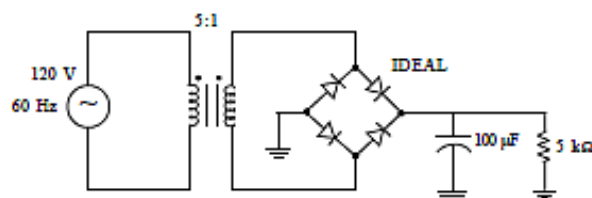- 3. Attempt any one part of the following: 10 x 1 = 10**
- Determine the DC load voltage and ripple voltage for the circuit as shown in figure.




b. With help of a neat schematic explain the Loaded Zener regulator.

**4. Attempt any *one* part of the following: 10 x 1 = 10**

- a. Discuss the working of a CRO with help of a neat block diagram. Explain how the frequency and phase are measured.
- b. Explain the working of a full wave bridge rectifier with waveforms.

**5. Attempt any *one* part of the following: 10 x 1 = 10**

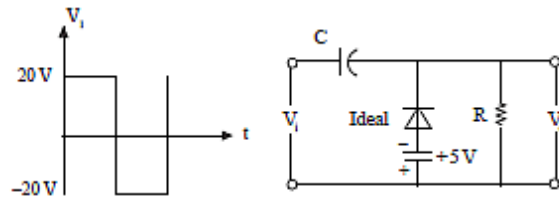- a. Sketch  $V_o$  of the following network shown in the given figure.



- b. What is the meaning of transistor biasing? Draw a neat sketch and explain the base biasing of transistor in CE mode.

**6. Attempt any *one* part of the following: 10 x 1 = 10**

- a. Explain trans-conductance. Also explain how JEET can be used as shunt switch and series switch.
- b. Draw the basic structure of a CE BJT and explain its basic principle of operation with neat diagram along with its input and output characteristics.

**7. Attempt any *one* part of the following: 10 x 1 = 10**

- a. Draw and explain the block diagram of digital voltmeter systems.
- b. Explain the working of following:
  - i. Cathode ray tube
  - ii. Schottky Diode